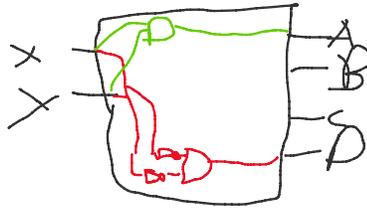


Day 3 (Jan 27th)

Monday, January 27, 2020 1:24 PM


2-to-4 Decoder:

X	Y	A	B	C	D
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0



3 to 8 Decoder:

X	Y	Z	S	C _o
			0	0
		1	0	
		1	0	
		0	1	
		1	0	
		0	1	
		0	1	
		1	1	

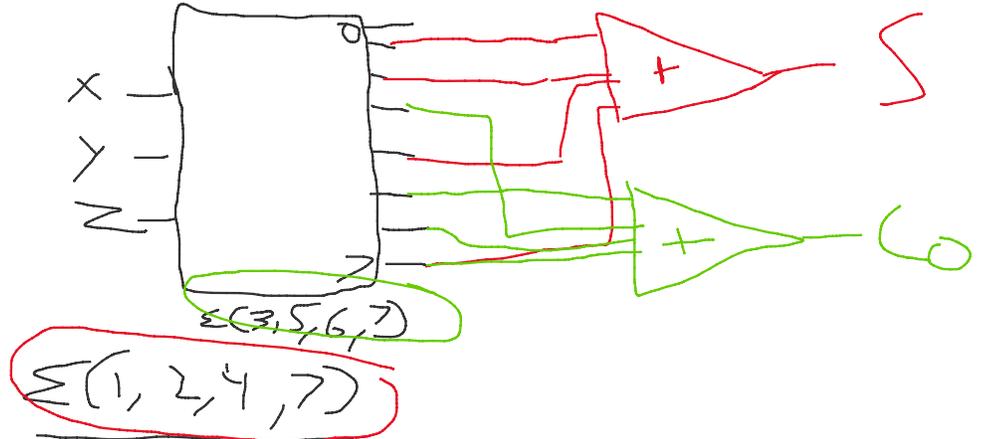

Priority Encoder:

For all zeros we don't care about the current output (because we shouldn't ever get all zeros)
 If C is 1 we don't care what D is so we can simplify the truth table
 If B is 1 we don't care about C or D
 If A is 1 we don't care about B, C or D

A	B	C	D	X	Y
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1

X Karnaugh Map:

		C	C	
	Y	0	0	
	1	1	1	B
A	1	1	1	B
A	1	1	1	
		D	D	

X: $A + B$ (the don't cares would be 0)


Y Karnaugh Map:

		C	C	
	X	0	1	
	0	0	0	B
A	1	1	1	B
A	1	1	1	
		D	D	

Y: $A'BC + A$ (the don't cares would be 0)

Multiplexer

S	I ₁	I ₀	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1

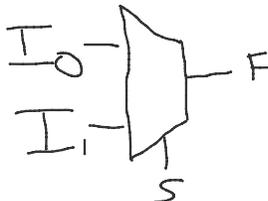


0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	1	

Basically Either copy over I_0 's column to F or I_1 's Column to F


			I_1	I_1	
	0	1	1	0	
S	0	0	1	1	
		I_0	I_0		

F: $S'I_0 + SI_1$

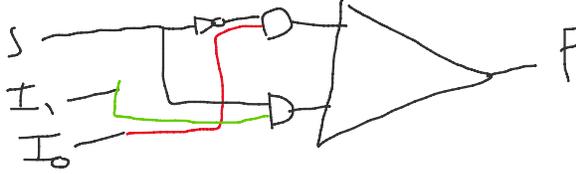

F=(1,2,6,7)

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

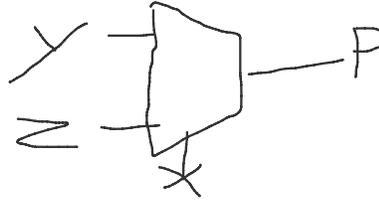


Selector bits are always the most significant bits (X in this single selector bit case)
Amount of Inputs are equal to $2^{\text{(Amount of Selector Bits)}}$

The Way to help visualize the multiplexor in the tables, you divide the Exclusive Or selector bit

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0

1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

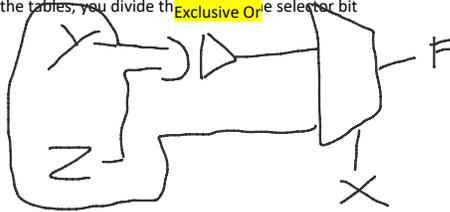

Two Selector Bits:

X	Y	Z	F
0	0	0	0
0	0	1	1

0	1	0	1
0	1	1	0

1	0	0	0
1	0	1	0

1	1	0	1
1	1	1	1

